
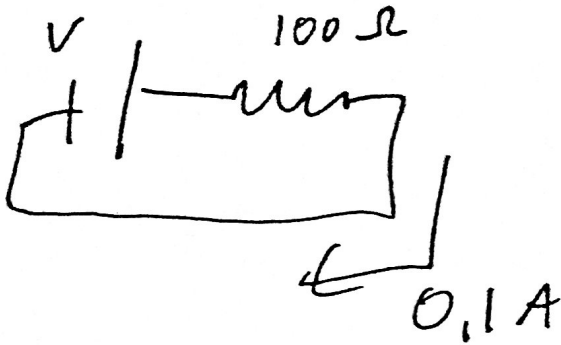


Classwork 5/31

1. Find the voltage of the battery

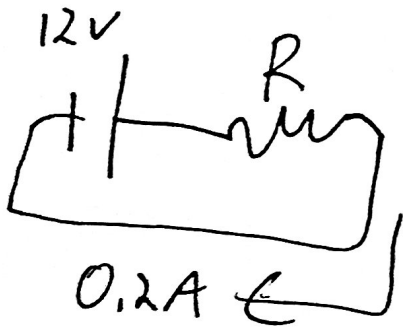

2. Find the resistance of the resistor



Ohm's Law

$$V = IR$$

Voltage = Current x Resistance