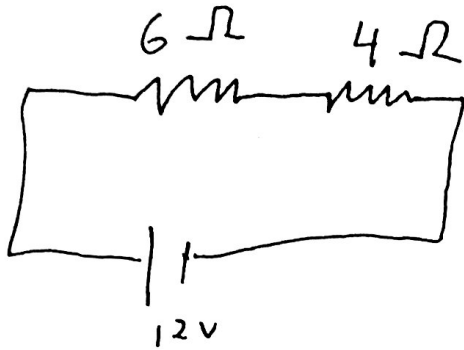



Class work 6-5

Find the equivalent resistance & the current flowing through each circuit.

1.



2.

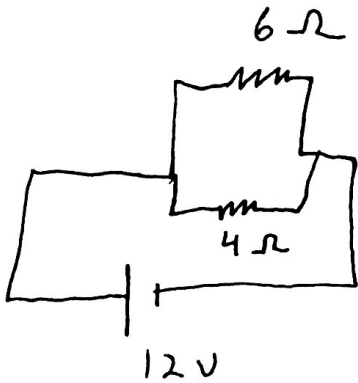

Series $R_{eq} = R_1 + R_2$

Parallel $\frac{1}{R_{eq}} = \frac{1}{R_1} + \frac{1}{R_2}$

Ohm's Law $V = IR$